



UNIVERSITY OF VOCATIONAL TECHNOLOGY
Faculty of Training Technology
Bachelor of Technology in Information & Communication Technology
(Multimedia & Web, Software, Network) 2015 / 2016 (B1)
Year I – Semester- I Examination - September -2015

Computer Architecture & Operating System IT10301

Instructions : Answer five questions only

Duration : 03 Hours

1.
 - 1.1. Simplify the following expressions using Boolean algebra.
 - a. $AB + A(B+C) + B(B+C)$ (Marks 05)
 - b. (Marks 05)
 - 1.2. Draw logic circuits for the following Boolean equations.
 - a. (Marks 05)
 - b. (Marks 05)
 - 1.3. Prove the following Boolean algebra laws using truth tables.
 - a. (Marks 05)
 - b. (Marks 05)
2.
 - 2.1. Draw the truth table and the logic diagram of 2-4 Decoder. (Marks 10)
 - 2.2. Compare and contrast Multiplexer and De- Multiplexer. (Marks 10)
3.
 - 3.1. Explain the function of the D-flip flop using a diagram. (Marks 06)
 - 3.2. Discuss the advantages of Memory a cell over a D- flip flop as a memory device. (Marks 06)
 - 3.3. Compare and contrast semiconductor memory and magnetic memory. (Marks 08)

4.
 - 4.1. Design a logic circuit to store two bits of memory using a detail logic diagram of a memory cell. (Marks 10)
 - 4.2. Design a logic circuit to store 32 bits (word length 8 bits) using a block diagram of a memory chip with both the capacity and word length of four bit. (Marks 10)

5.
 - 5.1. Briefly explain the instruction set of a micro processor. (Marks 10)
 - 5.2 Briefly explain the fetch and executing cycle. (Marks10)

6.
 - 6.1. Briefly explain the functions of an operating system. (Marks 10)
 - 6.2 Briefly explain the process management in an operating system. (Marks10)